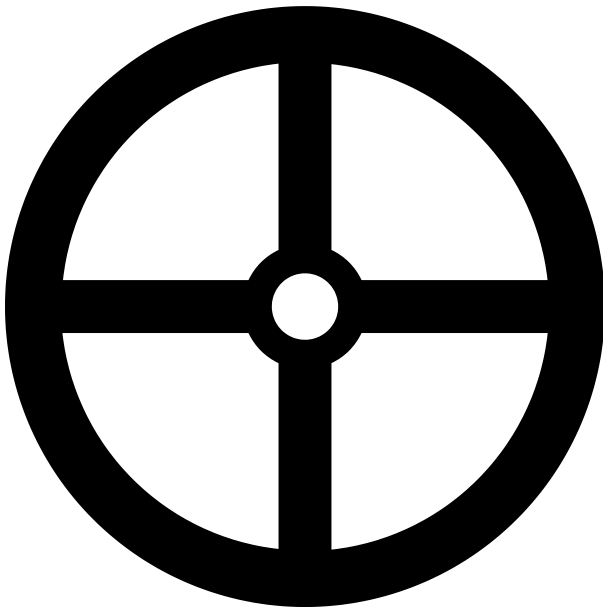


Visualising current as a wheel



Current : 0.0A

Voltage : 0.0V



☐ Generate Sine Wave

Select Circuit type:

- ☒ Pure Resistive
- ☐ Pure Inductive
- ☐ RL Circuit

Circuit Constants

Inductance : 1H

Resistance : 5Ω